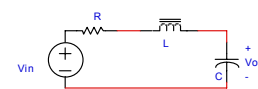



Overview of Laplace Solutions, Transfer Functions, Impedance, and Frequency Response

Charlie Sullivan
ENGS 22

Note: All of this works only on LTI systems!



Laplace Method

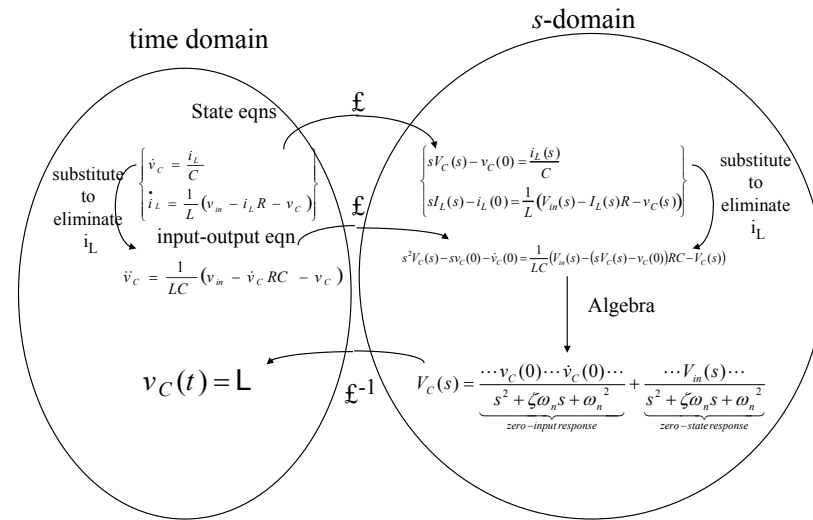

Two observations on Laplace Solution:

$$V_C(s) = \underbrace{\frac{\dots v_C(0) \dots \dot{v}_C(0) \dots}{s^2 + \zeta\omega_n s + \omega_n^2}}_{\text{zero-input response}} + \underbrace{\frac{\dots V_{in}(s) \dots}{s^2 + \zeta\omega_n s + \omega_n^2}}_{\text{zero-state response}}$$

With constant, step or zero input, Responses are all $C + A_1 e^{p_1 t} + A_2 e^{p_2 t} + A_3 e^{p_3 t} + \dots$
Characterize by roots of denominator, $\{p_1, p_2, p_3, \dots\}$
Real roots \rightarrow exponentials
Complex roots \rightarrow complex exponentials (damped oscillations) describe with ζ, ω_n


This is total response for zero init. condits. Note that it can be written:

$$V_{out}(s) = \frac{\dots}{s^2 + \zeta\omega_n s + \omega_n^2} V_{in}(s)$$

Thus, for zero init. condits., $V_{out}(s) = H(s) \cdot V_{in}(s)$
and $v_{out}(t) = \mathcal{F}^{-1}\{H(s) \cdot V_{in}(s)\}$
Note that this does **not** mean $v_{out}(t) = \{h(t) \cdot v_{in}(t)\}$

Poles of $H(s) \Leftrightarrow$ response with step or constant input


Obtaining $H(s)$ (for zero init condits)

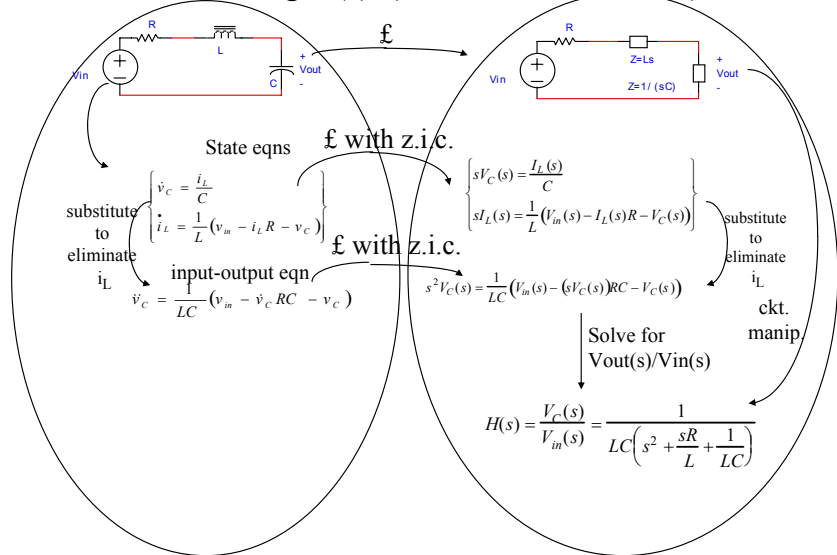


Response using $H(s)$

For zero init. condits., $V_{out}(s) = H(s) \cdot V_{in}(s)$ $v_{out}(t) = \mathcal{L}^{-1} \{H(s) \cdot V_{in}(s)\}$

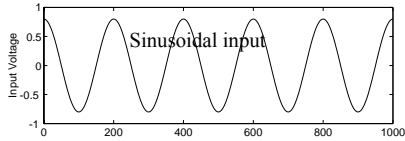
Example: $H(s)$ from last page, plus $v_{in}(t) = u(t) \cos(\omega t)$
(cosine that turns on at time zero)



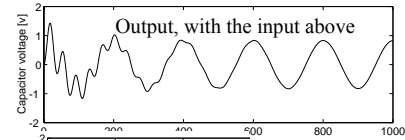Result: Response reflecting roots of $H(s)$ plus response reflecting input frequency. The former decays leaving sinusoidal steady state.



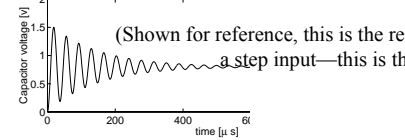Calculating this complete response gets nasty, so nasty, that actually....



I used a numerical solution:

lrcplot.m

```
% Plot response of LRC circuit
% (described in lrc.m)
% to sinusoidal input.
% crs
[t,y]=ode45('lrc',[0,1e-3],[0;0]);
subplot(2,1,2)
plot(t*1e6,y(:,2))
big
ylabel('Capacitor voltage [v]')
xlabel('time [μs]')
subplot(2,1,1)
plot(t*1e6,0.8*cos(2*pi*5e3*t))
big
ylabel('Input Voltage')
```


lrc.m

```
function xd = lrc(t,x)
% Derivative function for
ode45
% LRC circuit
% C Sullivan
% states iL; Vc


% Set Parameters
R = 8; % ohms
C = 0.06e-6; % farads
L = 575e-6; % Henries
v0 = 0.8; % volts
w = 2*pi*5e3;

A = [-R/L -1/L; 1/C 0];
B = [1/L; 0];
xd = A*x + B*v0*cos(w*t);
```

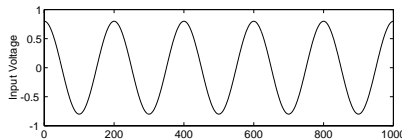What good is $H(s)$ with sinusoidal input?



Ignore this

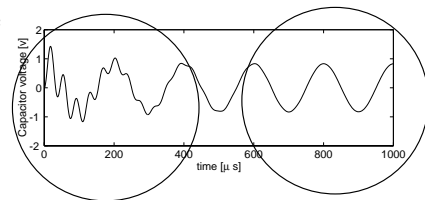

Look at this:
“Sinusoidal Steady-State”

need:
 G (one in this case)
 ϕ (zero in this case)

Amazingly simple result:

$$G = |H(j\omega)|$$

$$\phi = \angle(H(j\omega))$$

Evaluating $H(j\omega)$

- Use MATLAB as a complex-number calculator.
- Get qualitative idea
- Evaluate $|H(j\omega)|$ and $\angle(H(j\omega))$ algebraically
- Express $H(s)$ as $H(s) = \frac{(s-z_1)(s-z_2)L}{(s-p_1)(s-p_2)(s-p_3)L}$

z is a zero, a place on the s -plane where $H \rightarrow 0$ (plotted o)

p is a pole, where $H \rightarrow \infty$ (plotted x)

- Now plug in $s = j\omega$ $H(j\omega) = \frac{(j\omega-z_1)(j\omega-z_2)L}{(j\omega-p_1)(j\omega-p_2)(j\omega-p_3)L}$
- Each term is a distance (a complex vector distance on the s -plane) between p or z and $j\omega$, a point on the imaginary axis at a height corresponding to the input frequency we want to study.
- If we want to know $|H(j\omega)|$, then all we need is

$$|H(j\omega)| = \frac{|j\omega-z_1| \cdot |j\omega-z_2| \cdot L}{|j\omega-p_1| \cdot |j\omega-p_2| \cdot |j\omega-p_3| \cdot L}$$

Each term in this is just the length of a distance vector.

